

Recitation 4

Date: Feb 24, 2013

For practice using Logism, try building circuits for the following truth tables in Logism!

p	q	f(p, q)
T	T	F
T	F	F
F	T	F
F	F	T

p	q	r	f(p, q, r)
T	T	T	F
T	F	T	F
F	T	T	F
F	F	T	T
T	T	F	F
T	F	F	T
F	T	F	F
F	F	F	T


Problem 4.1

You may recall learning that the *AND*, *OR*, and *NOT* gates are, together, capable of expressing all of logic. Put another way, if you can build each of the truth tables for *AND*, *OR*, and *NOT* using some combination of expressions, then you can build any truth table using that combination.

- Prove that we **cannot** express all logic gates using only the *XOR* gate.
- Prove that we **cannot** express all of logic using only the \rightarrow expression.
- Prove that we **can** express all of logic using only the \rightarrow expression and *NOT* gates.

Note: To represent a particular logic gate, you may only use the inputs specified for that gate.

Problem 4.2

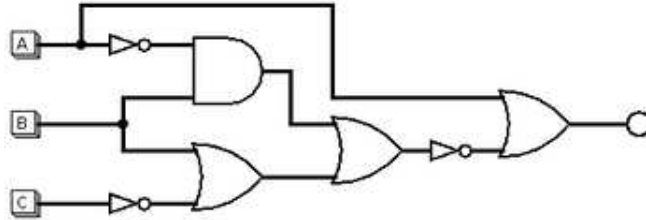

This circuit looks a little overcomplicated.

- Write out the expression for the circuit
- Simplify the expression
- Verify that the expressions are equivalent using truth tables
- Draw the circuit for the simplified expression